

P01 Report

Deepak Raj Gopal

February 2019

Chapter 1

Theoretical part

1.1 Circuit Calculation

Theoretical calculation of the circuit $V_1=1.1V-0.275$

$R_1=2ohm$ $R_2=2ohm$

$$VR = (R \times VT) / RT$$

$$VR_1 = (R_1 \times V_1) / RT = 1.1V$$

$$VR_2 = (R_2 \times V_2) / RT = -0.275V$$

Table 1.1:

- Table for resistance and voltage

V1	1.1
R1	2ohm
R2	2ohm
UR1	1.1V
UR2	-0.275V

 


Figure 1.1: Electrical Circuit Diagram
-0.275

Chapter 2

Practical part

Practical Calculation

2.1 Working on with GEDA programs'

2.1.1 'Working with gschem'

Figure 2.1: Circuit Diagram created in gschem


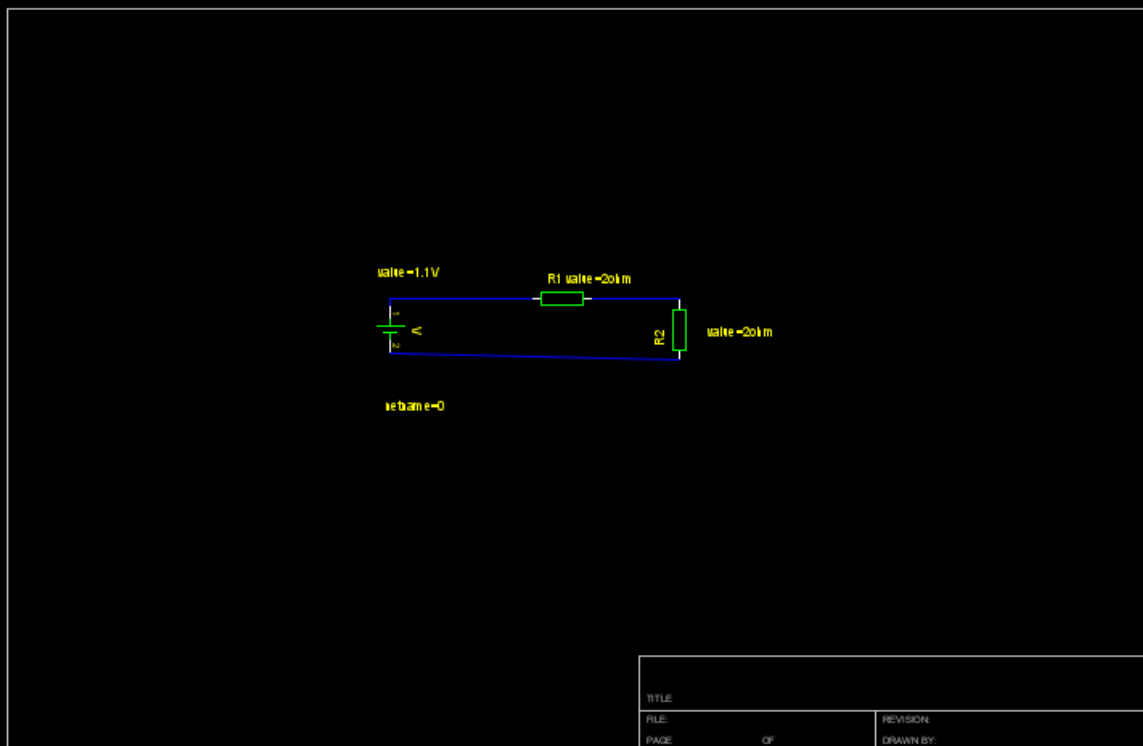


Figure 2.2: The plotted graph after using ngspice

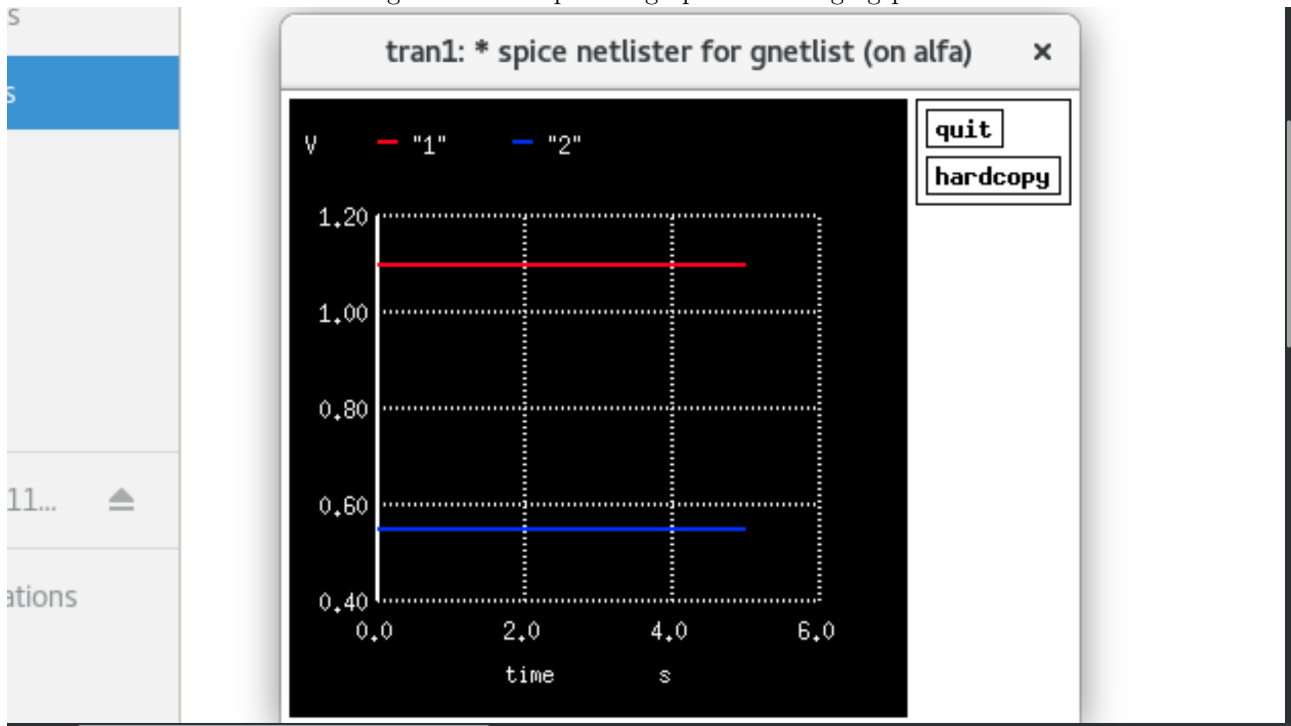

2.1.2 'Work with gnetlist'

